

J. Zhou 2015-02-16

DC parameters of Four-port network

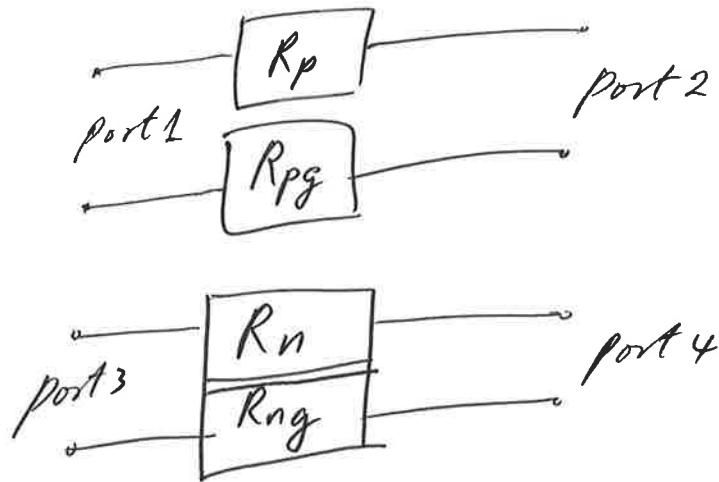


Fig1. Four-port network at DC

(eight terminal)
Fig1 depicts a four-port network at DC. It consists of R_p , R_{pg} , R_n , R_{ng} ~~resistor~~ resistances.

where R_p and R_n ~~refere~~ are the resistances of two separate power or signal nets and R_{pg} and R_{ng} are the DC resistance of the ground net, between port 1, port 2 and port 3 port 4


we wish to obtain the ~~the~~ S or Y parameters of the ~~net~~ four-port network at DC.

The Z parameter of such network doesn't exist, ~~but do~~ due to the lack of resistive path between power-ground or signal-ground

①

Section 1. Y parameter

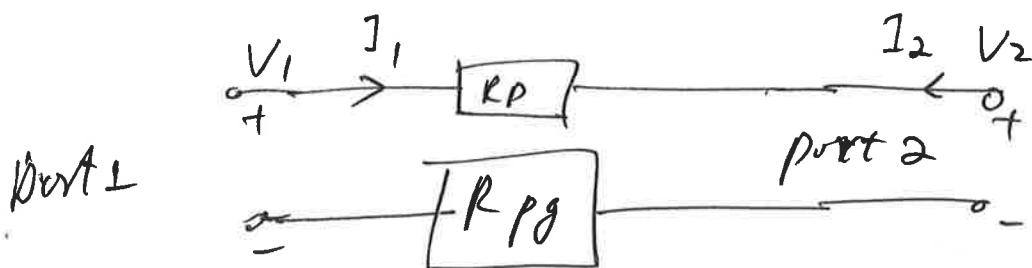~~the~~ Y parameter between port 1 and port 2



apply V_1 at port 1, short port 2, ($V_2 = 0$)
we have $I_1 = -I_2 = \frac{V_1}{R_p + R_{pg}}$

based on Y parameter definition:

$$I_1 / V_2 = 0 = Y_{11} V_1, \quad I_2 / V_2 = 0 = Y_{21} V_1$$

we have $Y_{11} = \frac{1}{R_p + R_{pg}}$

$Y_{21} = -\frac{1}{R_p + R_{pg}}$

Similarly apply V_2 at port 2 and set $V_1 = 0$

we have $I_2 = -I_1 = \frac{V_2}{R_p + R_{pg}}$

$$I_2 \Big|_{V_1=0} = Y_{22} V_2, \quad I_1 \Big|_{V_1=0} = Y_{12} V_2$$

we obtain:

$$Y_{22} = \frac{1}{R_p + R_{pg}}, \quad Y_{12} = -\frac{1}{R_p + R_{pg}}$$

$$Y = \frac{1}{R_p + R_{pg}} \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix}$$

note that ~~the~~ $\det(Y) = 0$, ~~and~~

this is caused by the fact I_1, I_2 are not independent

The four port Y matrix is

$$Y = \begin{bmatrix} Y_p & -Y_p & 0 & 0 \\ -Y_p & +Y_p & 0 & 0 \\ 0 & 0 & Y_n & -Y_n \\ 0 & 0 & -Y_n & Y_n \end{bmatrix}$$

where $Y_p = 1 / (R_p + R_{pg})$

$$Y_n = 1 / (R_n + R_{ng})$$

Section 2 S-parameter

The S-parameter of port 1, port 2 are given by eqns (301) (302) (303) (304)

in "network-analysis-05.pdf" on pg 31

~~$$S_{11} = 1$$~~

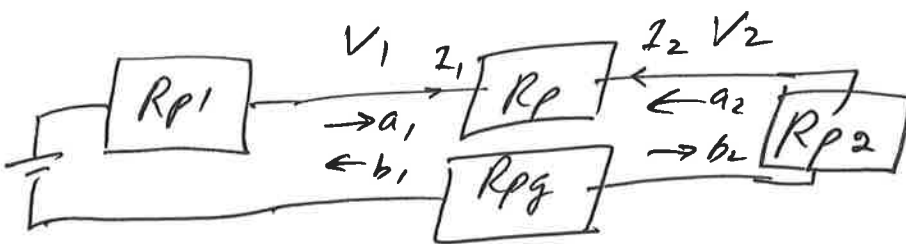


Fig. 2

$$\Sigma R_p = R_{p1} + R_p + R_{pg} + R_{p2}$$

where R_{p1} R_{p2} are ref impedances of port 1, port 2, respectively

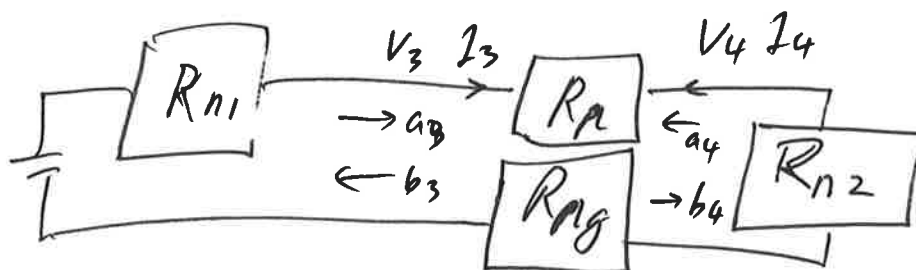


Fig. 3

$$\Sigma R_n = R_{n1} + R_n + R_{ng} + R_{n2}$$

$$S_{11} = 1 - \frac{2 R_{p1}}{\Sigma R_p}$$

$$S_{12} = S_{21} = \frac{2 \sqrt{R_{p1} R_{p2}}}{\Sigma R_p}$$

$$S_{22} = 1 - \frac{2 R_{p2}}{\Sigma R_p}$$

$$S_{33} = 1 - \frac{2 R_{n2}}{\Sigma R_n}$$

$$S_{34} = S_{43} = \frac{2 \sqrt{R_{n1} R_{n2}}}{\Sigma R_n}$$

$$S_{44} = 1 - \frac{2 R_{n2}}{\Sigma R_n}$$

$$S = \begin{bmatrix} S_{11} & S_{12} & 0 & 0 \\ S_{21} & S_{22} & 0 & 0 \\ 0 & 0 & S_{33} & S_{34} \\ 0 & 0 & S_{43} & S_{44} \end{bmatrix}$$

(The end)